 


# Computer Architecture ( VHDL coding) Lab

# Basic structure of VHDL programming

The full form of VHDL



There are two portion in VHDL coding.

1. **Entity part:** In entity part all inputs, outputs of a hardware circuit and their types are declared.
2. **Architecture part:** In architecture part the actual logic is defined.

## VHDL code

```
Entity part {  
  entity entity_name is  
    Port ( port name : in type;  
          port name : out type);  
  end entity_name;  
Architecture part {  
  architecture Behavioral of entity_name is  
  Begin  
  Actual logic;  
  end Behavioral;
```

For input it is in

Type is either bit or STD\_LOGIC


For output it is out

Bit represents either logic 0 or logic 1 only these two logic.  
STD\_LOGIC represent standard logic ( logic 0, logic1, Uninitialized(U),  
Don't care (X), High Impedance (Z) like different types of logic)
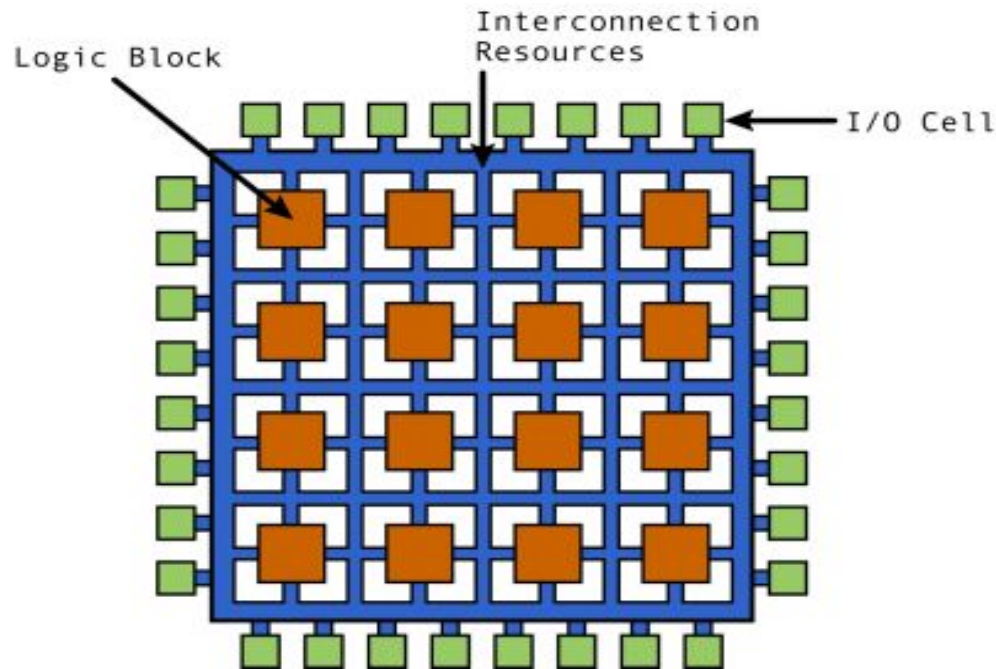
## FPGA (Field-Programmable Gate Array)

A **field-programmable gate array (FPGA)** is an integrated circuit designed to be configured by a customer or a designer after manufacturing.

Uses for FPGAs cover a wide range of areas—from equipment for video and imaging, to circuitry for computer, auto, aerospace, and military applications.



FPGA architecture

# FPGA architecture contd.

The three basic types of programmable elements for an FPGA

## **Configurable logic block (CLB):**

An individual CLB consists of a number of discrete logic components itself, such as look-up tables (LUTs) and flip-flops.

**I/O block:** Input/output blocks are the components through which data transfers in to and out of the FPGA.


## **Programmable interconnect:**

Programmable Interconnect Points (PIP) provide the routing paths used to connect the CLBs and inputs/outputs.

It is a CMOS transistor switch which can be turned on or off by using programming.

Logically these are nothing but MUX and DMUX.

# AND Gate

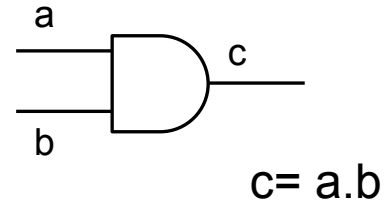

## VHDL code for AND Gate (Dataflow design):

entity andgate is

Port ( a, b : in bit;  
c : out bit);

end entity;


architecture Behavioral of andgate is

begin

c<=a AND b;

end Behavioral;

# OR Gate

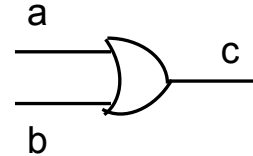

$$c = a + b$$

## VHDL code for OR Gate (Dataflow design):

entity orgate is

```
    Port ( a : in  STD_LOGIC;  
          b : in  STD_LOGIC;  
          c : out STD_LOGIC);
```

end orgate;


architecture Behavioral of orgate is

begin

```
c<=a OR b;
```

end Behavioral;

# XOR Gate

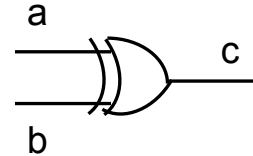

$$c = a \oplus b$$

## VHDL code for XOR Gate (Dataflow design):

entity xorgate is

```
    Port ( a : in  STD_LOGIC;  
          b : in  STD_LOGIC;  
          c : out STD_LOGIC);
```

end xorgate;


architecture Behavioral of xorgate is

begin

```
c<=a XOR b;
```

```
end Behavioral;
```

# Half Adder

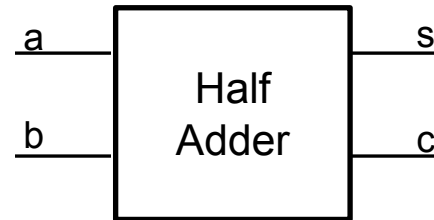

$$s = a \oplus b$$

$$c = a.b$$

## VHDL code for Half adder (Dataflow design):

entity HA is

Port ( a : in STD\_LOGIC;

b : in STD\_LOGIC;

s : out STD\_LOGIC;

c : out STD\_LOGIC);

end HA;

architecture Behavioral of HA is

begin


s<=a XOR b;

c<=a AND b;

end Behavioral;



# Full Adder

 

$$sf = af \oplus bf \oplus cin$$

$$cout = af.bf + bf.cin + cin.af$$

## VHDL code for Full Adder (Dataflow design):

entity FA is

```
Port ( af : in  STD_LOGIC;
      bf : in  STD_LOGIC;
      cin : in  STD_LOGIC;
      sf : out STD_LOGIC;
      cout : out STD_LOGIC);
```

end FA;

architecture Behavioral of FA is

Begin

```
sf<=af XOR bf XOR cin ;
```

```
cout<=(af AND bf) OR (bf AND cin) OR (cin AND af) ;
```

```
end Behavioral;
```

There are three types of design in VHDL code


- 1) Dataflow design
- 2) Structural design
- 3) Behavioral design

**1) Dataflow design:** This design is completely logic expression based.

**2) Structural design:** Here basic building blocks are used to design a new hardware circuit. Like function

**3) Behavioral design:** This design is completely truth table based.

# Full Adder using two Half Adder

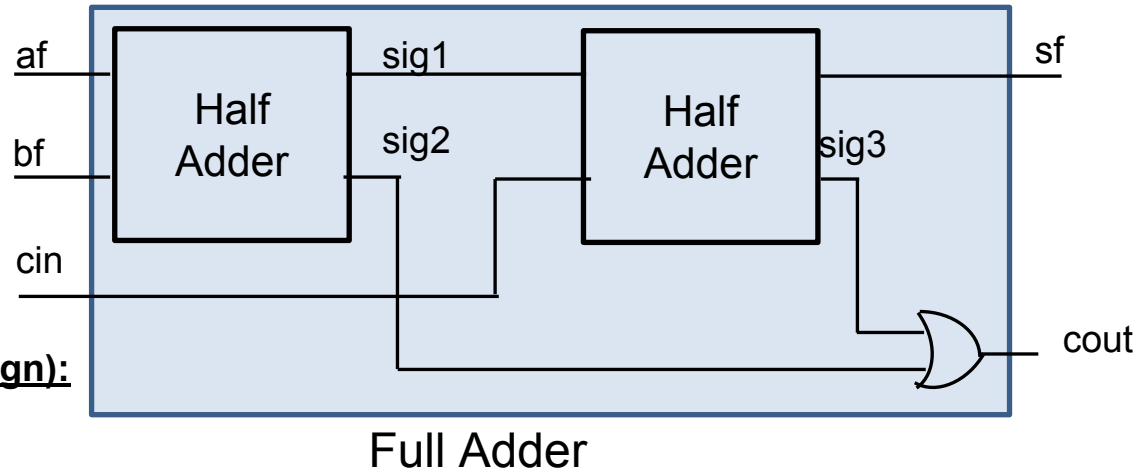

## VHDL code for Full Adder (Structural design):

entity FA is

```
Port ( af : in  STD_LOGIC;  
      bf : in  STD_LOGIC;  
      cin : in  STD_LOGIC;  
      sf : out STD_LOGIC;  
      cout : out STD_LOGIC);
```

end FA;

architecture Behavioral of FA is

component HA is

```
Port ( a : in  STD_LOGIC;  
      b : in  STD_LOGIC;  
      s : out STD_LOGIC;  
      c : out STD_LOGIC);
```

Component  
It is like a function  
prototype

end component;

```
signal sig1,sig2,sig3: STD_LOGIC;
```

Here sig1, sig2 and sig3 are intermediate input output which are called signal.

begin

```
HA1:HA port map(af,bf,sig1,sig2);
```


```
HA2:HA port map(sig1,cin,sf,sig3);
```

Components are calling here two times.

```
cout<=sig2 OR sig3;
```

```
end Behavioral;
```

# Ripple Carry Adder

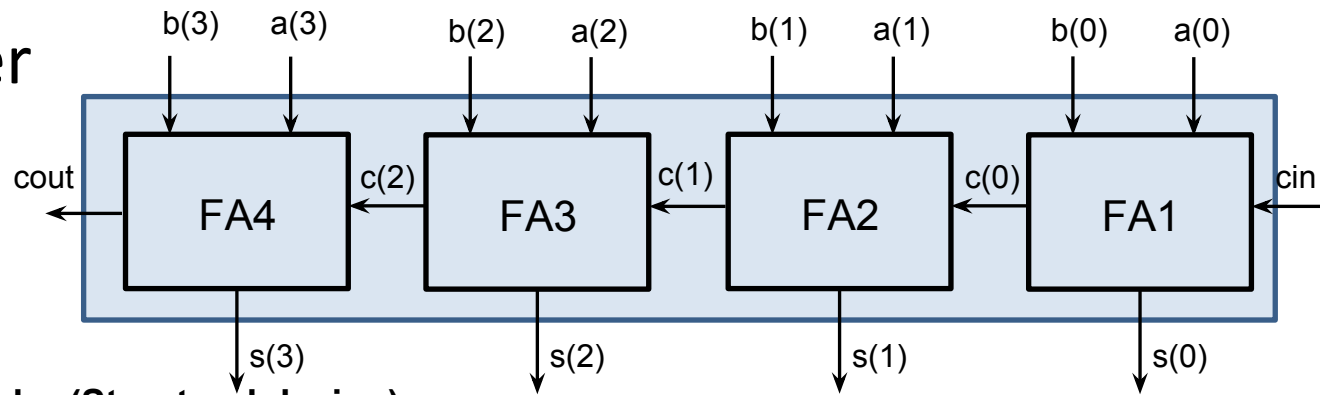

## VHDL code for Ripple Carry Adder (Structural design):

```
entity ripplecarryadder is
    Port ( a :in STD_LOGIC_VECTOR (3 downto 0);
          b : in STD_LOGIC_VECTOR (3 downto 0);
          cin : in  STD_LOGIC;
          s :out STD_LOGIC_VECTOR (3 downto 0);
          cout : out  STD_LOGIC);
```

```
end ripplecarryadder;
```

```
architecture Behavioral of ripplecarryadder is
```

```
component FA is
```

```
    Port ( af : in  STD_LOGIC;
          bf : in  STD_LOGIC;
          cin : in  STD_LOGIC;
          sf : out STD_LOGIC;
          cout : out STD_LOGIC);
```

```
end component;
```

```
signal c : STD_LOGIC_VECTOR (2 downto 0);
```


```
begin
```

```
    fa1:FA port map(a(0),b(0),cin,s(0),c(0));
    fa2:FA port map(a(1),b(1),c(0),s(1), c(1));
    fa3:FA port map(a(2),b(2),c(1),s(2), c(2));
    fa4:FA port map(a(3),b(3),c(2),s(3),cout);
```

```
end Behavioral;
```

Here VECTOR is used like an array.  
3 downto 0 means a is 4 bit binary number  
( a(3),a(2),a(1),a(0) )

# Adder-Subtractor composite unit

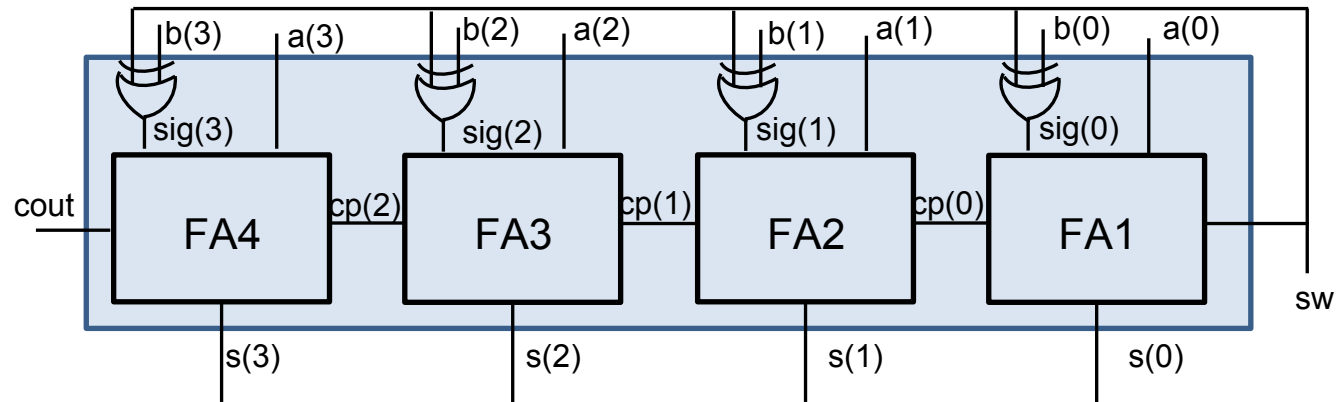

## VHDL code for Adder-Subtractor (Structural design):

```


entity addsub is
  Port ( a : in  STD_LOGIC_VECTOR (3 downto 0);
        b : in  STD_LOGIC_VECTOR (3 downto 0);
        sw : in  STD_LOGIC;
        s : out STD_LOGIC_VECTOR (3 downto 0);
        cout : out STD_LOGIC);
end addsub;

architecture Behavioral of addsub is
  component FA is
    Port ( af : in  STD_LOGIC;
          bf : in  STD_LOGIC;
          cin : in  STD_LOGIC;
          sf : out STD_LOGIC;
          cout : out STD_LOGIC);
  end component;

```

# Adder-Subtractor composite unit

contd.

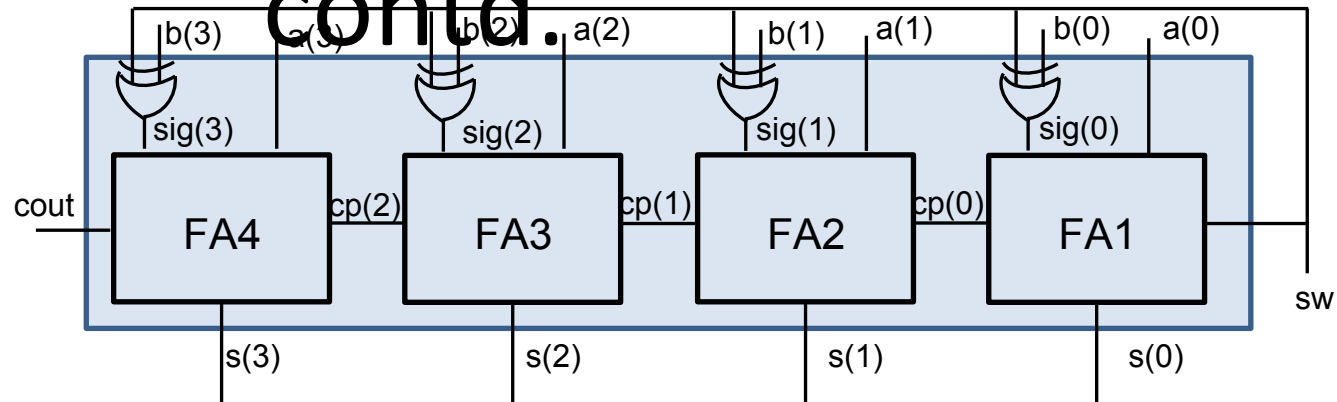

```

signal sig : STD_LOGIC_VECTOR (3 downto 0);
signal cp : STD_LOGIC_VECTOR (2 downto 0);
begin
sig(0)<=sw XOR b(0);
sig(1)<=sw XOR b(1);
sig(2)<=sw XOR b(2);
sig(3)<=sw XOR b(3);
fa1:FA port map(a(0),sig(0),sw,s(0),cp(0));
fa2:FA port map(a(1),sig(1),cp(0),s(1),cp(1));
fa3:FA port map(a(2),sig(2),cp(1),s(2),cp(2));
fa4:FA port map(a(3),sig(3),cp(2),s(3),cout);
end Behavioral;
    
```

# Multiplexer

## VHDL code for 4:1 Multiplexer (Behavioral design):

entity multiplexer is

Port ( I : in STD\_LOGIC\_VECTOR (3 downto 0);

S : in STD\_LOGIC\_VECTOR (1 downto 0);

O : out STD\_LOGIC);

end multiplexer;

architecture Behavioral of multiplexer is

begin

Process(I,S)

begin

case S is

when "00" => O<=I(0);

when "01" => O<=I(1);

when "10" => O<=I(2);

when "11" => O<=I(3);

when Others => O<='U';

end case;


end Process;

end Behavioral;

These parameters  
are called sensitivity list

Process block  
within process block execution  
is sequential

switch case

 

Truth Table

S(1)	S(0)	O
0	0	I(0)
0	1	I(1)
1	0	I(2)
1	1	I(3)

# Demultiplexer

## VHDL code for 1:4 Demultiplexer (Behavioral design):

entity demux is

Port ( I : in STD\_LOGIC;

S : in STD\_LOGIC\_VECTOR (1 downto 0);

O : out STD\_LOGIC\_VECTOR (3 downto 0));

end demux;

architecture Behavioral of demux is

begin

process(I,S)

begin

O<="UUUU";—— Here U means Uninitialized

case S is

when "00"=> O(0)<=I;

when "01"=> O(1)<=I;


when "10"=> O(2)<=I;

when others => O(3)<=I;

end case;

end process;

end Behavioral;

 

Truth Table


S(1)	S(0)	O(3)	O(2)	O(1)	O(0)
0	0	0	0	0	I
0	1	0	0	I	0
1	0	0	I	0	0
1	1	I	0	0	0



# Decoder
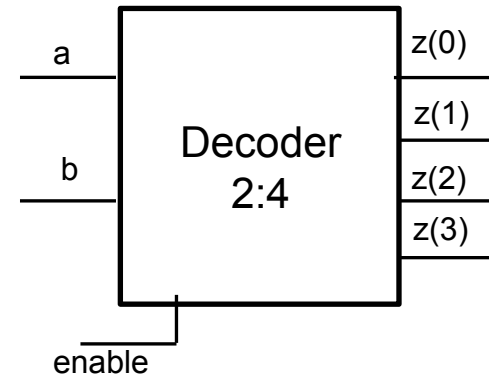
## VHDL code for 2:4 Decoder:

```
entity decoder is
  Port ( a : in  STD_LOGIC;
        b : in  STD_LOGIC;
        enable : in  STD_LOGIC;
        z : out STD_LOGIC_VECTOR (3 downto 0));
end decoder;
architecture Behavioral of decoder is
begin
  process(a,b,enable)
    variable abar,bbar:STD_LOGIC;—— Here abar, bbar are two variables
  begin
    abar:=NOT a;
    bbar:= NOT b;
    if enable='1'then
      z(0)<=abar AND bbar;
      z(1)<=abar AND b;
      z(2)<=a AND bbar;
      z(3)<=a AND b;
    else
      z<="UUUU";
    end if;
  end process;
end Behavioral;
```



Truth Table

a	b	z(3)	z(2)	z(1)	z(0)
0	0	0	0	0	1
0	1	0	0	1	0
1	0	0	1	0	0
1	1	1	0	0	0

$$z(0) = a' \cdot b'$$

$$z(1) = a' \cdot b$$

$$z(2) = a \cdot b'$$

$$z(3) = a \cdot b$$

# Difference between signal and variable

1. Signal is used to represent intermediate input output which has a real existence.  
Variable is used to store the value temporary and not really exist in the hardware circuit.
2. Assigning value to signal and variable is different.

```
signal s :STD_LOGIC;  
s<='1';  
variable v : STD_LOGIC;  
v:='1';
```

### VHDL code for Full Adder (Behavioral design):

```
entity fulbehaviour is
  Port ( a : in  STD_LOGIC;
        b : in  STD_LOGIC;
        cin : in  STD_LOGIC;
        s : out STD_LOGIC;
        cout : out STD_LOGIC);
end fulbehaviour;
architecture Behavioral of fulbehaviour is
begin
  process(a,b,cin)
    variable sw: std_logic_vector(2 downto 0);
  begin
    sw(0):=cin;
    sw(1):=b;
    sw(2):=a;
    case sw is
      when "000" => s<='0';cout<='0';
      when "001" => s<='1'; cout<='0';
      when "010" => s<='1'; cout<='0';
      when "011" => s<='0'; cout<='1';
      when "100" => s<='1'; cout<='0';
      when "101" => s<='0'; cout<='1';
      when "110" => s<='0'; cout<='1';
      when others => s<='1'; cout<='1';
    end case;
  end process;
end Behavioral;
```

Truth Table of Full Adder

a	b	cin	s	cout
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

# Multiplication Using ADD and shift method

M = 8

M = 1000

Q = 0110

Q = 6

A	Q	Size	Comment
0000	0110	4	initialize
0000 1000	0011	3	Right Shift A and Q
1000	0011	3	A+M
0100 1000	0001	2	Right Shift A and Q
1100	0001	2	A+M
0110	0000	1	Right Shift A and Q
0011	0000	0	Right Shift A and Q

Product = 0011 0000


# VHDL code for 4 bit binary multiplier

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.STD_LOGIC_arith.ALL;
use IEEE.STD_LOGIC_unsigned.ALL;

entity binary_multiplier is
    Port ( m : in  STD_LOGIC_VECTOR (3 downto 0);
          q : in  STD_LOGIC_VECTOR (3 downto 0);
          r : out STD_LOGIC_VECTOR (7 downto 0));
end entity;

architecture multiplier of binary_multiplier is
begin
    process(m,q)
        variable acc: std_logic_vector(8 downto 0);
        variable multiplicand:std_logic_vector(4 downto 0);
    begin
        acc(8 downto 4):="00000";
        acc(3 downto 0):=q;
        multiplicand:='0' & m;
        for i in 1 to 4 loop
            if acc(0)='1' then
                acc(8 downto 4):=acc(8 downto 4)+ multiplicand;
            end if;
            acc:='0' & acc(8 downto 1);
        end loop;
        r<= acc(7 downto 0);
    end process;
end multiplier;
```

# Restoring Division Flow chart

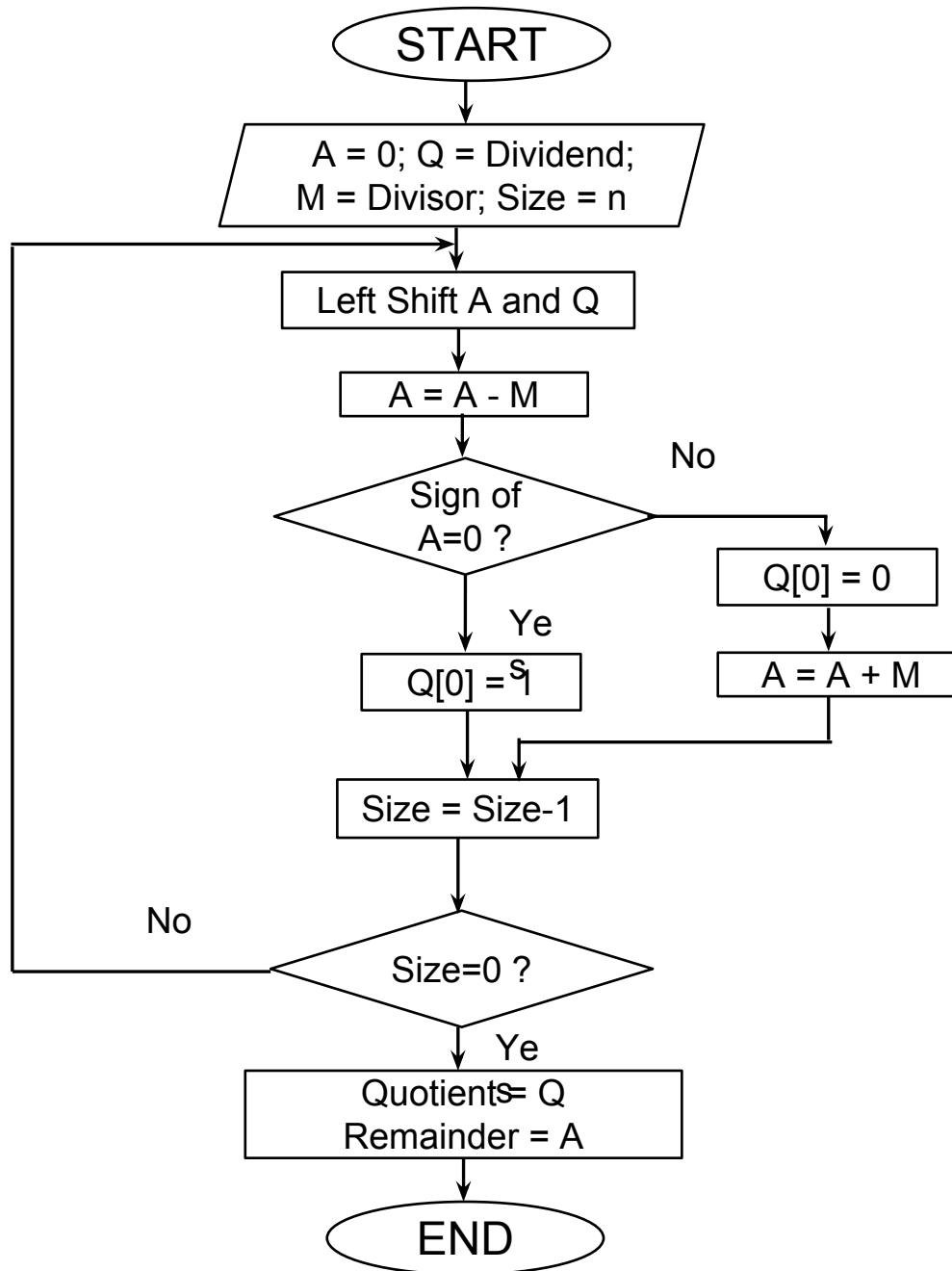

# Restoring Division Example

M = 3, Q = 7

Q =

M = 0011

-M = 1101

A	Q	Size	Comment
0111			
0000	011	4	initialize
0000	11 <input type="checkbox"/>	4	Left Shift A and Q
1101	1		
1101	11 <input type="checkbox"/>	4	A=A-M
0011	1		Set Q[0]=0 and
0000	111 <input type="checkbox"/>	3	A=A+M
0001	11 <input type="checkbox"/> <input type="checkbox"/>	3	Left Shift A and Q
1101			
111	11 <input type="checkbox"/> <input type="checkbox"/>	3	A=A-M
0011			Set Q[0]=0 and
0001	11 <input type="checkbox"/> <input type="checkbox"/>	2	A=A+M
0011	1 <input type="checkbox"/> <input type="checkbox"/> <input type="checkbox"/>	2	Left Shift A and Q
1101			
0000	1 <input type="checkbox"/> <input type="checkbox"/> <input type="checkbox"/>	2	A=A-M
0000	1 <input type="checkbox"/> <input type="checkbox"/> <input type="checkbox"/> <input type="checkbox"/>	1	Set Q[0]=1
0001	<input type="checkbox"/> <input type="checkbox"/> <input type="checkbox"/> <input type="checkbox"/>	1	Left Shift A and Q
1101			
111	<input type="checkbox"/> <input type="checkbox"/> <input type="checkbox"/> <input type="checkbox"/>	1	A=A-M
0011			Set Q[0]=0 and
0001	<input type="checkbox"/> <input type="checkbox"/> <input type="checkbox"/> <input type="checkbox"/>	0	A=A+M
Remainder	Quotient		

# VHDL code for 4 bit restoring division

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.STD_LOGIC_arith.ALL;
use IEEE.STD_LOGIC_unsigned.ALL;

entity division is
    Port ( d : in  STD_LOGIC_VECTOR (3 downto 0);
          m : in  STD_LOGIC_VECTOR (3 downto 0);
          q : out STD_LOGIC_VECTOR (3 downto 0);
          r : out STD_LOGIC_VECTOR (3 downto 0));
end division;


architecture Behavioral of division is
begin
    process(d,m)
        variable ac:std_logic_vector(7 downto 0);
        variable Mbar:std_logic_vector(3 downto 0);
    begin
        Mbar:=not m;
        ac:="0000" & d;
```

```
        for i in 1 to 4 loop
            ac(7 downto 0):=ac(6 downto 0) & 'U';
            ac(7 downto 4):=ac(7 downto 4)+Mbar+"0001";

            if ac(7)='1' then
                ac(0):='0';
                ac(7 downto 4):=ac(7 downto 4)+m;
            else
                ac(0):='1';
            end if;
        end loop;
        q<=ac(3 downto 0);
        r<=ac(7 downto 4);
    end process;
end Behavioral;
```



# 4 bit Arithmetic Unit

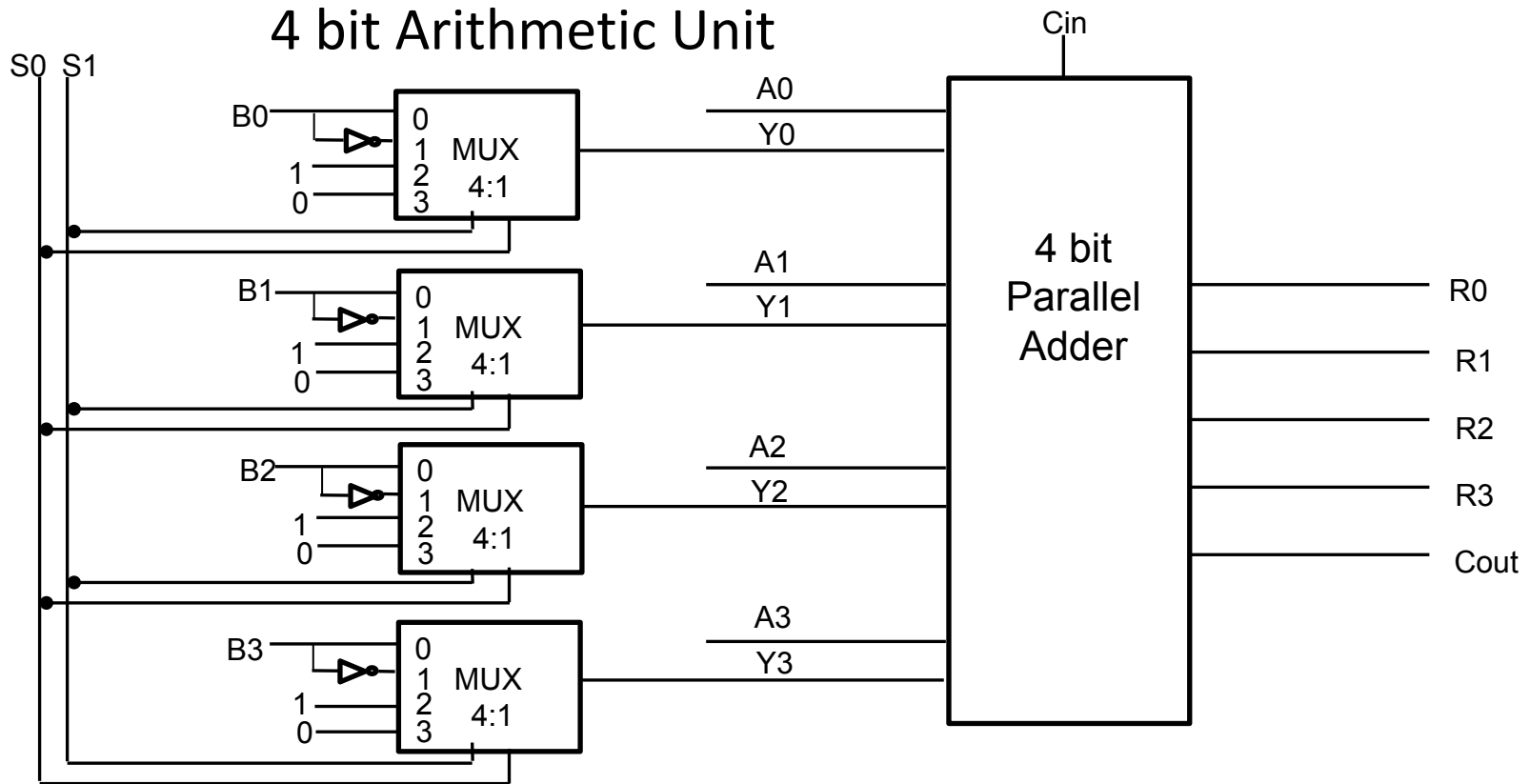

S1	S0	Cin	Y	$F=A+Y+Cin$	Operation
0	0	0	B	$F=A+B$	Addition
0	0	1	B	$F=A+B+1$	Addition with carry
0	1	0	$\bar{B}$	$F=A+\bar{B}$	Subtraction with borrow
0	1	1	$\bar{B}$	$F=A+\bar{B}+1$	Subtraction
1	0	0	-1	$F=A-1$	Decrement
1	0	1	-1	$F=A$	Transfer
1	1	0	0	$F=A$	Transfer
1	1	1	0	$F=A+1$	Increment

# VHDL code for 4 bit Arithmetic Unit

```
library ieee;
use ieee.std_logic_1164.all;
use ieee.std_logic_arith.all;
use ieee.std_logic_unsigned.all;
entity alu4bit is
  port(a,b : in std_logic_vector(3 downto 0);
        s: in std_logic_vector(1 downto 0);
        cin: in std_logic;
        r: out std_logic_vector(3 downto 0);
        cout : out std_logic );
end alu4bit;
architecture arch1 of alu4bit is
begin
  process(a,b,s,cin)
    variable sw: std_logic_vector(2 downto 0);
    variable a1,b1,r1: std_logic_vector(4 downto 0);
    begin
```

```
      sw(0):=cin;
      sw(1):=s(0);
      sw(2):=s(1);
      a1:='0' & a;
      b1:='0' & b;case sw is
        when "000" => r1:=a1+b1;
        when "001" => r1:=a1+b1+'1';
        when "010" => r1:=a1+not(b1);
        when "011" => r1:=a1+not(b1)+'1';
        when "100" => r1:=a1-'1';
        when "101" => r1:=a1;
        when "110" => r1:=a1;
        when "111" => r1:=a1+'1';
        when others=> r1:="UUUUUU";
      end case;
      r<=r1(3 downto 0); cout<=r1(4);
    end process;
  end arch1;
```

# VHDL code for designing 128 x 8 bit RAM chip

```
library ieee;
use ieee.std_logic_1164.all;
use ieee.std_logic_arith.all;
use ieee.std_logic_unsigned.all;
entity memory1 is
port(clk: in std_logic ;
cs : in std_logic ;
r : in std_logic ;
w : in std_logic ;
clr: in std_logic;
abus:in std_logic_vector(6 downto 0);
dbus:inout std_logic_vector(7 downto 0));
end memory1;
```

```
architecture arch1 of memory1 is
type ma is array(0 to 127) of
std_logic_vector(7 downto 0);
signal mem : ma;
begin
process(clk)
begin
if(rising_edge(clk) and cs='1') then
    if w='1' then
        mem(conv_integer(unsigned(abus)))<=dbus;
    end if;
    if r='1' then
        dbus<=mem(conv_integer(unsigned(abus)));
    end if;
    if clr='1' then
        for i in 0 to 127 loop
            mem(i)<="UUUUUUUU";
        end loop;
    end if;
end if;
end process;
end arch1;
```

Thank You